1. The voltage V (in volts) across a circuit is given by $V = IR$ (Ohm's Law), where I is the current (in amps) flowing through the circuit and R is the resistance (in ohms). If we place two circuits, with resistance R_1 and R_2, in parallel, then their combined resistance R is given by

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

Suppose the current is 2 amps and increasing at 10^{-2} amp/sec and R_1 is 3 ohms and increasing at 0.5 ohm/sec, while R_2 is 5 ohms and decreasing at 0.1 ohm/sec. Calculate the rate at which the voltage is changing.